

8. (3 points) Given that each XOR gate has a delay of A ns, each AND gate has a delay of B ns, and each OR gate has a delay of C ns, what is the propagation delay of the worst case path in an N bit ripple carry adder? Assume that the delays between the elements are close enough that the worst case path is the one that contains the most elements along it.

$$\text{XOR} + A$$

$$\text{AND} \cdot (B + C)$$

N bit ripple carry

$$N * (B + C) + A$$