

Homework 1

The pdf you submit must look exactly like this with the answers and all supporting works shown on the the page with the question.

Last Name

Waheed

First Name

Muhammaad

Student ID

912741428

Partner Last Name

Magno

Partner First Name

Mathew

Partner Student ID

913366789

1. (5 points) Use Boolean Algebra to prove that

$$(\bar{A} * B * \bar{C}) + (\bar{A} * B * C) + (A * \bar{B} * \bar{C}) + (A * \bar{B} * C) + (A * B * \bar{C}) + (A * B * C) = (A + B) * (B + C)$$

$$(\bar{A} \cdot B \cdot \bar{C}) + (\bar{A} \cdot B \cdot C) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C) + (A \cdot B \cdot \bar{C}) + (A \cdot B \cdot C) = (A + B) \cdot (B + C)$$

Taking $(\bar{A} \cdot B)$ common

$$(\bar{A} \cdot B)(\bar{C} + C) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C) + (A \cdot B \cdot \bar{C}) + (A \cdot B \cdot C) = (A + B) \cdot (B + C)$$

Taking $(A \cdot B)$ common and putting $(\bar{C} + C) = 1$

$$(\bar{A} \cdot B)(1) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot B)(\bar{C} + C) \overset{+(A \cdot B \cdot C)}{=} (A + B)(B + C)$$

Putting $(\bar{C} + C) = 1$

$$(\bar{A} \cdot B)(1) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot B)(1) \overset{+(A \cdot B \cdot C)}{=} (A + B) \cdot (B + C)$$

$$(\bar{A} \cdot B) + (A \cdot B) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot B \cdot C) = (A + B) \cdot (B + C)$$

taking C and A common

$$(\bar{A} \cdot B) + (A \cdot B) + (A \cdot C)(\bar{B} + B) = (A + B) \cdot (B + C)$$

Setting $(B + \bar{B}) = 1$

$$(\bar{A} \cdot B) + (A \cdot B) + (A \cdot C) = (A + B) \cdot (B + C)$$

Taking B common

$$B(\bar{A} + A) + (A \cdot C) = (A + B) \cdot (B + C)$$

By $\bar{A} + A = 1$

$$B + (A \cdot C) = (A + B) \cdot (B + C)$$

$$(B + A) \cdot (B + C) = (A + B) \cdot (B + C)$$

Rearranging

$$(A + B) \cdot (B + C) = (A + B) \cdot (B + C)$$

$$LHS = RHS$$

2. (3 points) Prove that $A \text{ XOR } B = A \cdot \bar{B} + \bar{A} \cdot B$

Truth table for $A \text{ XOR } B$ Truth table for expression $A \cdot \bar{B} + \bar{A} \cdot B$


A	B	$A \oplus B$
0	1	0
0	0	1
1	1	1
1	0	0

A	B	\bar{A}	\bar{B}	$A \cdot \bar{B}$	$\bar{A} \cdot B$	$A \cdot \bar{B} + \bar{A} \cdot B$
0	0	1	1	0	0	0
0	1	1	0	0	1	1
1	0	0	1	1	0	1
1	1	0	0	0	0	0

Both Sides are equal

$$\therefore, A \text{ XOR } B = A \cdot \bar{B} + \bar{A} \cdot B$$

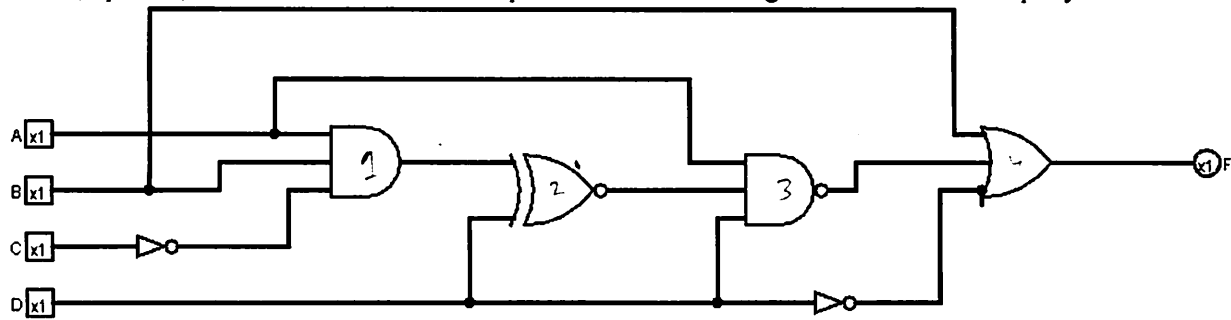3. (3 points) Write the function that represents the following circuit. Do not simplify.



$$1 = A \cdot B \cdot \bar{C}$$

XOR \oplus

$$2 = D$$

AND \sim

$$3 = (A \cdot D) \sim$$

$$4 = B + \bar{D}$$

Solution:

$$\left[((A \cdot B \cdot \bar{C}) \oplus D) \sim (A \cdot D) \sim B + \bar{D} \right]$$

4. Given the following truth table

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

1. (3 points) Write a function in SOP form that behaves according to the truth table. Do not simplify.

$$= (\bar{A}\bar{B}\bar{C}) + (\bar{A}\bar{B}C) + (\bar{A}B\bar{C}) + (A\bar{B}C) + (AB\bar{C})$$

2. (3 points) Write a function in POS form that behaves according to the truth table. Do not simplify.

$$= (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + C) \cdot (\bar{A} + \bar{B} + \bar{C})$$

5. (3 points each) For each of the following problems assume that the variables are $x_0 - x_{N-1}$, with x_0 representing the least significant bit and x_{N-1} the most significant. For example if we had an equation of 3 variables, $m_1 = \bar{x}_2 * \bar{x}_1 * x_0$ and $m_6 = x_2 * x_1 * \bar{x}_0$. For each of the following problems write each function in **both** its most simplified SOP and POS form. There are a total of 5 subquestions
1. $m_0 + m_1 + m_2$

x_0	x_1	output
0	0	1
0	1	1
1	0	1
1	1	0

$x_1 \backslash x_0$	0	1
0	1	1
1	1	0

POS: $\bar{x}_1 + \bar{x}_0$

SOP: $\bar{x}_1 + \bar{x}_0$

2. $M_0 * M_3 * M_4 * M_7$

x_0	x_1	x_2	out
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$x_0 \backslash x_1 \ x_2$	00	01	11	10
0	0	1	1	0
1	1	0	0	1

$$SOP: (x_1 \cdot \bar{x}_2) + (\bar{x}_1 \cdot x_2)$$

$$POS: (x_1 + x_2) \cdot (\bar{x}_1 + \bar{x}_2)$$

3. $m_4 + m_5 + m_7 + m_{12} + m_{13} + m_{15}$

	x_0	x_1	x_2	x_3	out
1	0	0	0	0	0
2	0	0	0	1	0
3	0	0	1	0	0
4	0	0	1	1	0
5	0	1	0	0	1
6	0	1	0	1	1
7	0	1	1	0	0
8	0	1	1	1	1
9	1	0	0	0	0
10	1	0	0	1	0
11	1	0	1	0	0
12	1	0	1	1	0
13	1	1	0	0	1
14	1	1	0	1	1
15	1	1	1	0	0
16	1	1	1	1	1

$x_2 x_3$	00	01	11	10
00	0	0	0	0
01	1	1	1	0
11	1	1	1	0
10	0	0	0	0

$$\text{POS} : (\bar{x}_2 + x_3) \cdot x_1$$

$$\text{SOP} : (x_1 \cdot \bar{x}_2) + (x_1 \cdot x_3)$$

4. $m_0 + m_3 + m_4 + m_8 + D_2 + D_5 + D_7 + D_{10} + D_{13} + D_{15}$

	x_0	x_1	x_2	x_3	OUT
1	0	0	0	0	1
2	0	0	0	1	0
3	0	0	1	0	d
4	0	0	1	1	1
5	0	1	0	0	1
6	0	1	0	1	d
7	0	1	1	0	0
8	0	1	1	1	d
9	1	0	0	0	1
10	1	0	0	1	0
11	1	0	1	0	d
12	1	0	1	1	0
13	1	1	0	0	0
14	1	1	0	1	d
15	1	1	1	0	0
16	1	1	1	1	d

$x_2 x_1$	00	01	11	10
00	1	0	1	d
01	1	d	d	0
11	0	d	d	0
10	1	0	0	d

SOP: $(\bar{x}_0 \cdot \bar{x}_2 \cdot \bar{x}_3) + (x_2 \cdot \bar{x}_0 \cdot \bar{x}_1) + (\bar{x}_2 \cdot \bar{x}_3 \cdot \bar{x}_1)$

POS: $(\bar{x}_3 + x_2) \cdot (\bar{x}_3 + \bar{x}_2) \cdot (\bar{x}_2 + x_3) \cdot (\bar{x}_1 + \bar{x}_3)$

5. $m_1 + m_3 + m_7 + m_9 + m_{11} + m_{15} + m_{17} + m_{19} + m_{25} + m_{27} + D_4 + D_6 + D_{12}$
 $+ D_{14} + D_{16} + D_{18} + D_{20} + D_{22} + D_{24} + D_{26} + D_{28} + D_{30}$

	x_0	x_1	x_2	x_3	x_4	Out
1	0	0	0	0	0	
2	0	0	0	0	1	
3	0	0	0	1	0	
4	0	0	0	1	1	
5	0	0	1	0	0	
6	0	0	1	0	1	
7	0	0	1	1	0	
8	0	0	1	1	1	
9	0	1	0	0	0	
10	0	1	0	0	1	
11	0	1	0	1	0	
12	0	1	0	1	1	
13	0	1	1	0	0	
14	0	1	1	0	1	
15	0	1	1	1	0	
16	0	1	1	1	1	
17	1	0	0	0	0	
18	1	0	0	0	1	
19	1	0	0	1	0	
20	1	0	0	1	1	
21	1	0	1	0	0	
22	1	0	1	0	1	
23	1	0	1	1	0	
24	1	0	1	1	1	
25	1	1	0	0	0	
26	1	1	0	0	1	
27	1	1	0	1	0	
28	1	1	0	1	1	
29	1	1	1	0	0	
30	1	1	1	0	1	
31	1	1	1	1	0	
32	1	1	1	1	1	

$x_3 x_2$	00	01	11	10
00	0	1	1	0
01	1	0	1	1
11	1	0	1	1
10	0	1	1	0

$x_3 x_2$	00	01	11	10
100	x	1	1	x
101	x	0	0	x
111	x	0	0	x
110	x	1	1	x

$x_3 x_2$	00	01	11	10
00	0	1	1	0
01	1	0	1	1
11	1	0	1	1
10	0	1	1	0

$x_3 x_2$	00	01	11	10
100	x	1	1	x
101	x	0	0	x
111	x	0	0	x
110	x	1	1	x

SOP: $x_1 \cdot \bar{x}_2 + x_3 \cdot x_2 \cdot \bar{x}_0$

POS: $x_1 (x_3 + \bar{x}_2) (x_0 + x_2)$